

CSE 260M / ESE 260

Intro. To Digital Logic & Computer Design

Bill Siever
&
Michael Hall

This week

- Hw 4A posted later today / early tomorrow
 - Shorter than 3B; Not complex, but working with new tools, which may take time or review.
- Next Tues
 - Catch-up and Exam review (in class)
 - Expecting to have TA-led Exam review Tues
- Next Thurs: Exam 1 at class time

Studio 3B: Space Use


- n states
- ~ 8 Gates / Flip-flop (Via in-class approach)
- Assume simple approaches for decoding

ENCODING	GATES FOR STORAGE	GATES FOR DECODING	TOTAL (SPACE) GROWTH
BINARY	$8 \cdot \text{ceil}(\log_2(n))$	Likely n product terms of $\sim \log_2(n)$ variables	$\sim 8 \cdot \log_2(n) + n \cdot \log_2(n)$ $= O(n \log_2(n))$
ONE-HOT	$8 \cdot n$	0	$\sim 8n$ $= O(n)$


Rough Graph

Dff Time Parameters

 
- t_{pcq} : Propagation delay from Clock to Q (pcq)
- t_{ccq} : Contamination delay from C to Q (ccq)



Review: Moore Machine Structure

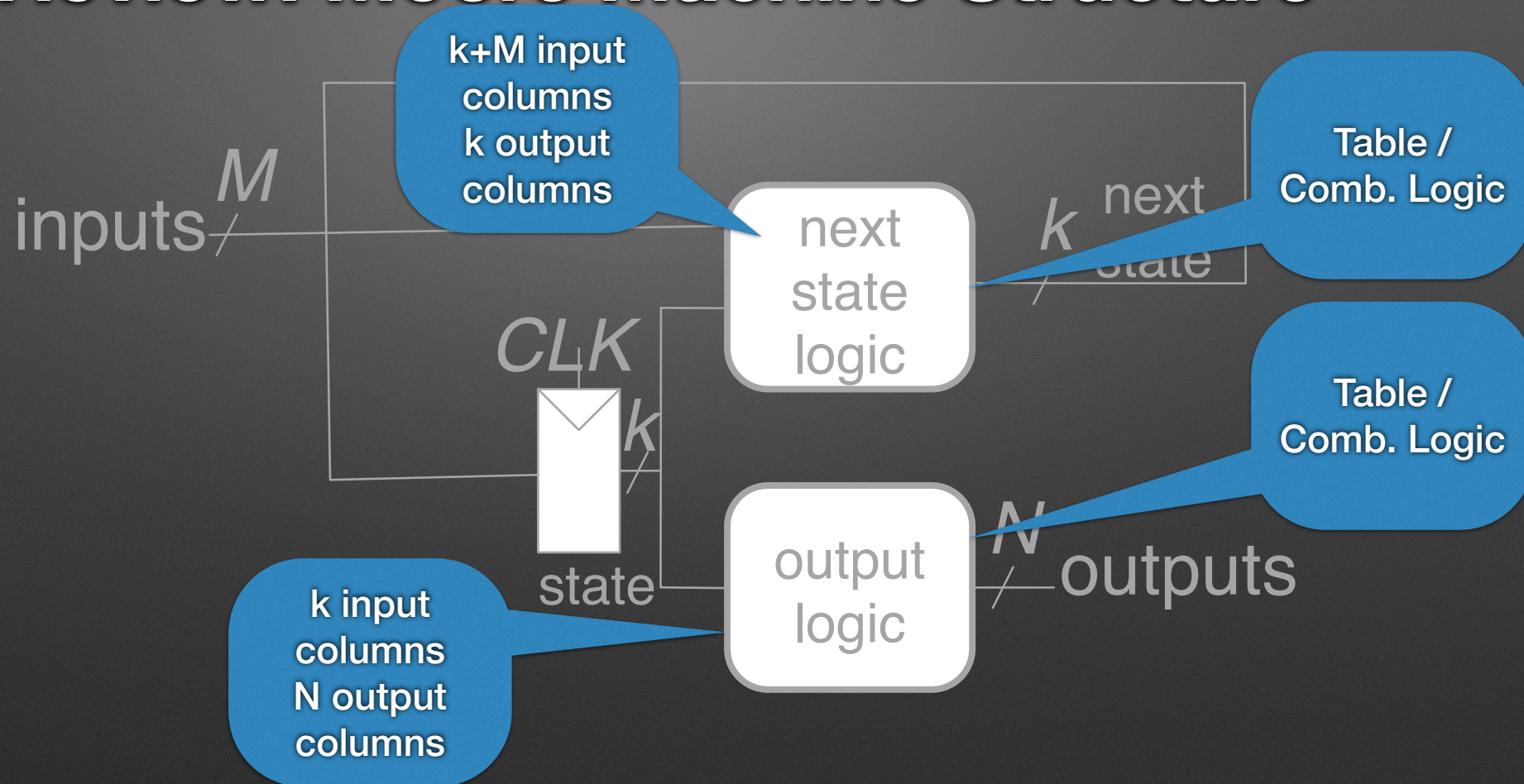

D-Flip-Flop Clock

 


https://www.ni.com/docs/en-US/bundle/ni-hsdio/page/hsdio/fedge_trigger.html

Studio 3B Review


- D-FF Model
 - NOR oscillation - Why?
 - *Important:* Circuits are composed of continually, concurrently executing elements!
- D-Latch Setup / Hold: Shaping waveforms and measuring around clock
 - Demonstrates concept, but shouldn't be measured empirically in practice!
(Rely on data sheets in this class)

Dff: Setup & Hold Time

 


Setup Time Constraint

 - Max time from R1 through CL
- R2's input needs to be stable t_{setup} before clock



Review: Moore Machine Structure

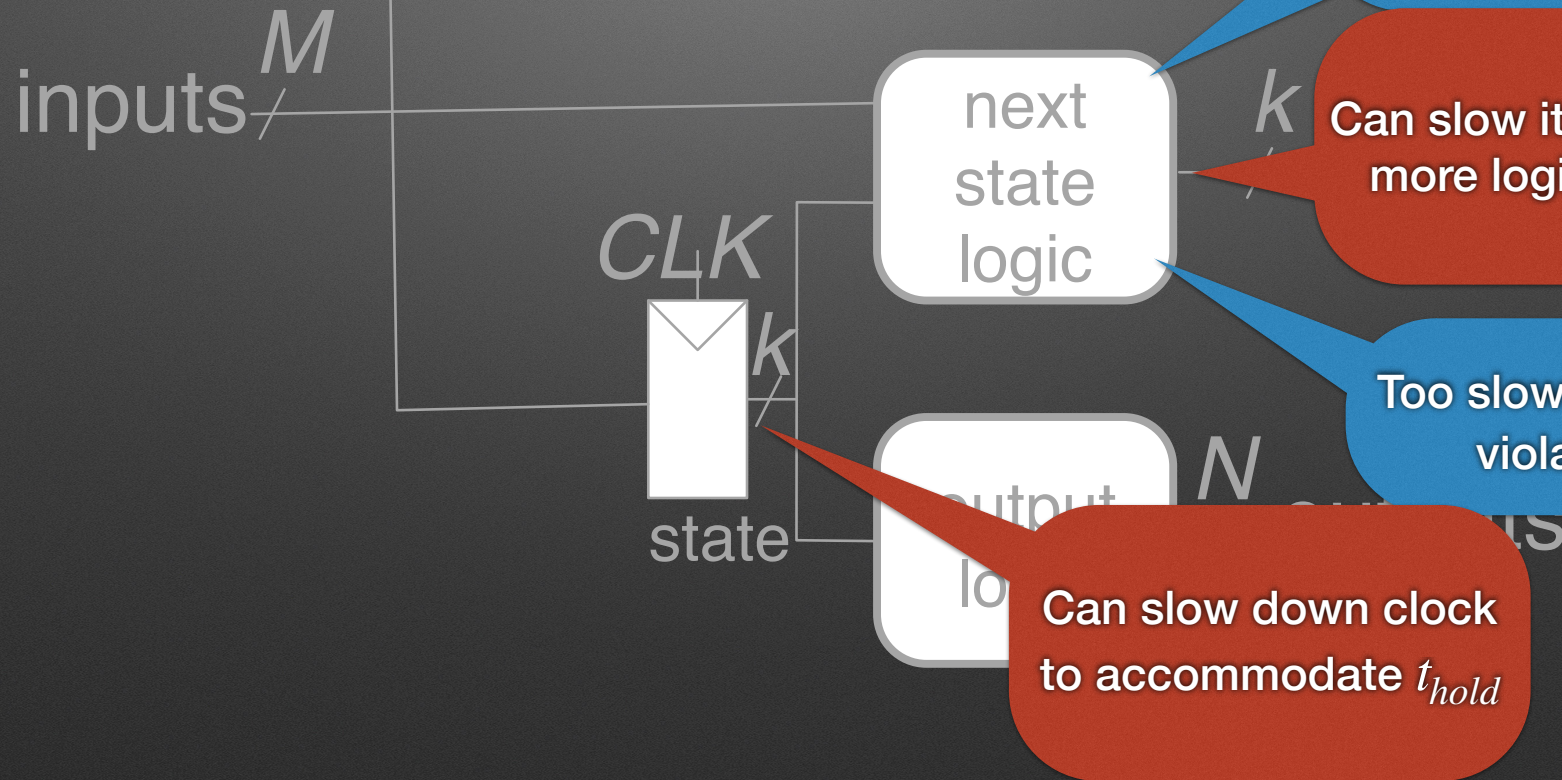

Chapter 4

Hardware Description Languages (HDLs)

- Specifies logic function only
- Computer-aided design (CAD) tool produces or synthesizes the optimized gates
- Most commercial designs built using HDLs

VHDL

- VHDL 2008
- Developed in 1981 by the Department of Defense
- IEEE standard (1076) in 1987
- Updated in 2008 (IEEE STD 1076-2008)

Questions this week:
Verilog?
VHDL?
Both?

**Questions this week:
Verilog?**

Both?

We will use Verilog

Not VHDL

(System) Verilog

- Developed in 1984 by Gateway Design Automation
- IEEE standard (1364) in 1995
- Extended in 2005 (IEEE STD 1800-2009)


HDL

- A HDL is not a computer program.
- A HDL is not a computer program!
- A HDL is *not* a computer program!
- A HDL is not a computer program!
- A HDL is **NOT** a computer program!


HDL

- HDL is a way to *describe* hardware
- HDLs typically can describe hardware in different ways
- HDLs describe hardware in modules

(System) Verilog Module Example

 


(System) Verilog Module Example

 


```
module example(input  logic a, b, c,  
               output logic y);  
    // module body goes here  
endmodule
```

 Input & Output
are like the Pins
On chips or in
JLS



HDL: Structural (Verilog)

 

```
module nand3(input logic a, b, c
             output logic y);
    logic n1; // internal signal

    and my_and(n1, a, b, c); // instance of and3
    not my_inverter(y, n1); // instance of inv
endmodule
```


Example & Tour of Environment

(System) Verilog

- Case sensitive
- Identifiers follow rules like in programming languages
 - Ex: 2inputGate not allowed, but gateWithTwoInputs is.
- Whitespace ignored
- C/Java Style comments:
 - // Comment to end of line
 - /*
Block Comment
*/

(System) Verilog

- Basic logic operators
 - Binary: $\&$, $|$, \wedge
 - Unary: \sim

HDL: Structural (Verilog)

```
module nand3(input  logic a, b, c
             output logic y);
    logic n1;                // internal signal

    and  my_and(n1, a, b, c); // instance of and3
    not  my_inverter(y,n1);   // instance of inv
endmodule
```


HDL: Structural (Verilog) (Without named instances)

```
module nand3(input  logic a, b, c
             output logic y);
    logic n1;           // internal signal

    and(n1, a, b, c);  // instance of and3
    not(y, n1);        // instance of inv
endmodule
```


HDL: Behavioral (Verilog)


```
module nand3(input  logic a, b, c
             output logic y);
    assign y = ~(a & b & c);
endmodule
```


(System) Verilog

- Multi-bit values: Array-like notation with bit ordering:
`logic [7:0] a;`
- Multi-bit reductions by pre-fix notation on multi-bit values
`assign y = &a;`

(System) Verilog

 - Conditionals via Ternary operator (? :)



```
module mux2(input logic [3:0] d0, d1,  
            input logic s,  
            output logic [3:0] y);  
    assign y = s ? d1 : d0;  
endmodule
```


Example

Operator Precedence

~	NOT
*, /, %	mult, div, mod
+, -	add, sub
<<, >>	shift
<<<, >>>	arithmetic shift
<, <=,	comparison
==, !=	equal, not equal
&, ~&	AND, NAND
^, ~^	XOR, XNOR
, ~	OR, NOR
? :	ternary

Number Formats

Number	# Bits	Base	Decimal	Stored
3'b101	3	binary	5	101
'b11	unsized	binary	3	00...0011
8'b11	8	binary	3	00000011
8'b1010_1011	8	binary	171	10101011
3'd6	3	decimal	6	110
6'o42	6	octal	34	100010
8'hAB	8	hexadecimal	171	10101011
42	Unsized	decimal	42	00...0101010

Verilog Bit Manipulations

- Subscripting and grouping

```
assign y = {a[2:1], {3{b[0]}}, a[0], 6'b100_010};
```

- Underscores can be used for clarity

Questions

- What about the exam????
- Will we use a HDL?
- [Which HDL?]
- How big will our circuits/computers get?
- What's synthesis? Are there things that can't be synthesized?
- Is my degree worth it? (I think mine was. Your mileage may vary...)